DEVELOPMENT OF SPECTRUM ANALYZER SYSTEM

Project report submitted by JOANNA TSERKEZOU

In part satisfaction of the award of DIPLOMA OF TECHNICIAN ENGINEER in Electrical Engineering of the Higher Technical Institute, Cyprus.

Project Supervisor: Mr. D. Lamprianides

Lecturer in Electical

Engineering, H.T.I.

Type of project: Individual
Group

Project number: E/855

June 1993



SUMMARY

A simplified diagram is shown for a typical spectrum analyzer, superheterodyne receiver, the spectrum analyzer is electronically tunable by applying an adjustable saw-tooth voltage ramp to a voltage tuned local oscillator (VTO), The same saw-tooth voltage ramp is applied simultaniously to the horizontal deflection plates of the CRT, to form the frequency axis of the display. The input signal is mixed with a signal from VTO, the output of the mixer is amplified, detected and then applied to the vertical plates of the Cathod Ray Tybe. Thus the vertical deflection is proportional to the amplitude of the input signal.

For an input signal Fs, the VTO frequency is tuned so that Fvto - Fs= Fif

When this equation is satisfied the input signal is deflected and displayed on the CRT.

Furthermore by slowly sweeping the full saw-tooth voltage the VTO sweeps through its frequency range and the output of the mixer will be a wide range of frequencies, but the IF amplifier will pass only those frequencies within its passband.

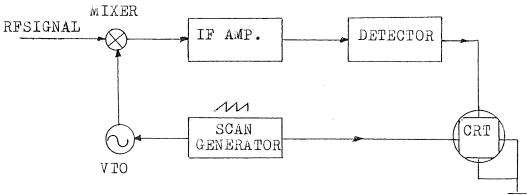


Figure 1. Simplified Spectrum Analyzer Block Diagram

CONTENTS

AGENOVIT DOG DE DUTIG	PAGE
ACKNOWLEDGEMENTS	I
SUMMARY	III
INTRODUCTION	IV
&	
CHAPTER 1	
INVESTIGATION OF VARIOUS TYPES OF SPECTRUM	
ANALYZERS.	1
1.1 REAL TIME SPECTRUM ANALYZER	2
1.2 SWEPT-TUNED SPECTRUM ANALYZER	4
1.3 SUPERHETERODYNE SPACTRUM ANALYZER	5
1.4 PROFESSIONAL STANDARDS REFERENCE	8
CHAPTER 2	
THE SPECTRUM ANALYZER BLOCK DIAGRAM	
2.1 FUNCTION	14
2.1 FUNCTION 2.2 BLOCK DIAGRAM	17
2.2 BLOCK DIAGRAM	1 [
CHAPTER 3	
THE POWER SUPPLY	
3.1 FUNCTION	19
3.2 CIRCUIT DIAGRAM	24
3.3 TESTING - RESULTS	21
3.4 INSTRUMENTS REQUIRED	21
CHAPTER 4	
THE MARKER GENERATOR	
4.1 FUNCTION	22
4.2 CIRCUIT DIAGRAM	24
4.3 TESTING	25
4.4 INSTRUMENTS REQUIRED	25
4.5 TROUBLESHOOTING	26
4.6 RESULTS & WAVEFORMS	27

CHAPTER 5	
THE SWEEP GENERATOR	
5.1 FUNCTION	28
5.2 CIRCUIT DIAGRAM	31
5.3 TESTING - CALIBRATION	32
5.4 INSTRUMENTS REQUIRED	35
5.5 CALCULATIONS	36
5.6 RESULTS & WAVEFORMS	38
CHAPTER 6	
THE VIDEO AMPLIFIER	
6.1 FUNCTION	39
6.2 CIRCUIT DIAGRAM	41
6.3 TESTING - CALIBRATION	42
6.4 INSTRUMENTS REQUIRED	43
6.5 TROUBLESHOOTING	43
6.6 RESULTS & WAVEFORMS	44
CHAPTER 7	
THE RF BOARD	
7.1 FUNCTION	45
7.2 CIRCUIT DIAGRAM	51
7.3 TESTING - CALIBRATION	52
7.4 INSTRUMENTS REQUIRED	55
7.5 TROUBLESHOOTING	55
CHAPTER 8	
COSTING	56
CHAPTER 9	
IMPROVEMENTS - GENERAL CONCLUSIONS	64
REFERENCES	
APPENDIX 1 PRINTED CCT BOARDS	
2 DRAWINGS-CIRCUITS	
3 DATA SHEETS	