SOUND CARD SYSTEM USING THE IBM-PC

BY:

ANTONIS ANTORKAS

Project Report submitted to the

Department of Electrical Engineering of the

Higher Technical Institute

Nicosia Cyprus

in partial fulfilment of the requirements

for the diploma of

TECHNICIAN ENGINEER ELECTRICAL ENGINEERING

Project Supervisor:

Mr S. Hadjioannou

External Accessor:

Mr F. Anastasios

1992



SOUND CARD SYSTEM USING THE IBM-PC

By: Antorkas Antonis

Summary:

The main objectives of this project were to design and construct an interface to the IBM-PC also an analog to Digital converter to sample analog signals and finally to write a program in either Pascal or Assembly to read the samples and to store them in a floppy disk or a hard disk.

The project relies on both hardware and software. The first four chapters are related to hardware. To be more specific the IBM-PC is emphasized and various signals are explained, an introduction to interfacing and the Sound Card Interfacing, the various Analog to Digital technics and the sampler of the Sound Card System and finally the Digital to Analog technics and the "reproduction stage" of the Sound Card System (the o/p DAC and the digital volume control).

The sixth chapter explains the various methods of implementing the software for the Sound Card System. Finally the software analysis, the environment and the listing of the program.

At the last chapter the various applications for this project are examined, testing is examined and the troubleshooting of the various parts of the Sound Card System. The costing and the comments and conclusions.

CONTENTS

ACKNO	WLEDGEMENTS	
SUMMA	RY	
INTRODUCTION		
Chapter 2	<u>1:</u>	
	GENERALLY ABOUT COMPUTERS BASIC PARTS OF AN IBM - PC 1.2.1 Central Processing Unit 1.2.2 Memory 1.2.3 Input & Output Devices or Ports 1.2.4 IBM-PC bus 1.2.5 Bus Signals 1.2.6 1.2.7 Bus Loading & Driving Capabilities	2 3 3 4 5 6 7 8
Chapter 2	2:	
Chapter		
	cing & Intel 8255 PPI	12
	GENERALLY ABOUT INTERFACING 2.1.1 I/O Peripheral Interfacing 2.1.2 Memory Mapped I/O Interfacing NTEL 8255 P.P.I BLOCK DIAGRAM OF SOUND CARD SYSTEM	13 13 13 16
		10
Chapter 3	<u>3:</u>	
ANAL	OG TO DIGITAL converter	
3.2	ANALOG TO DIGITAL CONVERSION 3.1.1 Sampling Theorem 3.1.2 Conversion Time ADC's ERRORS VARIOUS TYPES OF ADC's 3.3.1 Counter Type 3.3.2 Successive Approximation 3.3.3 Dual Slope	22 22 23 24 26 26 27 28

Contents

		Sound Card System using the	IBM-PC	
		3.3.4 Voltage to Frequency	30	
		3.3.5 Parallel or Flash	30	
	3.4	THE ZN 439	32	
		3.4.1 Sampling Frequency	33	
		3.4.2 Reference Voltage	33	
		3.4.3 Input Stage	35	
<u>Cha</u>	oter 4	<u>1:</u>		
DIC	-TT	AL TO ANALOG converter	36	
		DIGITAL TO ANALOG CONVERSION	37	
		VARIOUS TYPES OF DAC's	38	
		4.2.1 Binary Weighted Type	38	
		4.2.2 Ladder Type	39	
	4.3	THE DAC 0800	40	
		4.3.1 Why the DAC 08	40	
		4.3.2 Reference Voltage	40	
		4.3.3 Output Stage	43	
Chapter 5:				
Software Implementation			43	
001	5.1	GENERALLY ABOUT PROGRAMMING	44	
		5.1.1 The "TURBO VISION"	44	
		5.1.2 Object Oriented Programming	44	
	5.2		45	
		5.2.1 Various Methods of Software Sampling	45	
		5.2.2 An Example of an Assembly Sampling	16	
	5.3	Program TURBO PASCAL V6.0 PROGRAMMING	46 48	
	5.5	5.3.1 Sound Card System Requirements	40 49	
		5.3.2 Sound Card User's Guide	49	
		5.3.3 Program Listing	53	
<u>Chapter 6:</u>				
Δh	011 1	Sound Card System	54	
AU		APPLICATIONS	5 4 55	
	6.2		57	

COSTING COMMENTS & CONCLUSIONS

REFERENCES

6.3

6.4

60

61