

DESIGN, CONSTRUCTION, AND DEMONSTRATION
OF A
"DIGITAL AUDIO FREQUENCY RESPONSE
DISPLAY SYSTEM"

Project Report Submitted by
ZACHARIAS K. DEMETRIS

In part satisfaction of the award of
DIPLOMA OF TECHNICIAN ENGINEER
in Electrical Engineering of the
Higher Technical Institute, Cyprus.

Project Supervisor: Mr. D. Lamprianides
Lecturer in Electrical
Engineering, H.T.I.

Type of project: Individual
Group

June 1989



A B S T R A C T

This project deals with the research design, construction, calibration and testing of a digital frequency response display system.

Display is presented on a CRT screen. The instrument can give detail informations about the frequency response characteristics of an amplifier, an equilizer, any type of filter, or even a loudspeaker.

An investigation of the various types of spectrums is carried out in the first chapter including also a reference to professional standards.

A gradual presentation of the ideas assigning the selection of the constructed system is included in chapter 2. Moreover a reference to suggested system specifications is indicated in the introduction. A special reference is given in chapter 2.

In the following chapters explanation and analysis of the circuits used is done. Also testing and calibration results are presented. At the end of the report conclusions, test specifications, and demonstration informations are included.

C O N T E N T S

PAGE

| | | |
|------------------|---|-----|
| ACKNOWLEDGEMENTS | | I |
| ABSTRACT | | II |
| CONTENTS | | III |
| INTRODUCTION | | IV |
| | | |
| 1. | INVESTIGATION OF VARIOUS TYPES OF SPECTRUM ANALYZERS. | 1 |
| 1.1 | Multiple filter analyzer | 2 |
| 1.2 | Swept filter analyzer | 2 |
| 1.3 | Superheterodyne spectrum analyzer | 4 |
| 1.4 | Frequency Response Display System FRDS | 7 |
| 1.5 | Professional standards reference | 7 |
| | | |
| 2. | SPECIFICATIONS OF SELECTED SYSTEM AND BASIC BLOCK DIAGRAM | 8 |
| 2.1 | Frequency Response Display System FRDS | 9 |
| 1 | Principle of operation - Block diagram | 9 |
| 2 | Reference to scope settings | 10 |
| 3 | Reference to scope linearity | 10 |
| 2.2 | Digital Audio FRDS | 11 |
| 1 | Selection of audio ranges study | 11 |
| 2 | Selection of display system instead of an analyst | 11 |
| 3 | Selection of mode operation | 11 |
| 4 | Selection of 8-bits-Reference to resolution accuracy | 11 |
| 5 | Principle of operation-Functional Block diagram | 11 |
| | | |
| 3. | 8-BIT-DIGITAL RAMP GENERATOR MODULE | 15 |
| 3.1 | Function | 16 |
| 3.2 | Block diagram - Operation | 16 |
| 3.3 | Circuit diagram - Operation - Horizontal Scanning | 16 |

| | | |
|-------|---|--------|
| 3.3.1 | Analytical circuit explanation - Materials function | 18 |
| 3.4 | Supply requirements | 20 |
| 3.5 | Testing | 20 |
| 1 | Instruments required | 20 |
| 2 | Results - Characteristic curves | 20 |
| 3 | Calibration procedure - TEST POINTS | 22 |
| 4 | Comments - Conclusions | 23 |
| 4. | SINEWAVE GENERATOR MODULE | 24 |
| 4.1 | Function | 25 |
| 4.2 | Block diagram - Operation | 25 |
| 4.3 | Circuit diagram - operation | 25 |
| 4.3.1 | Analytical cct explanation-Materials function | 29 |
| 4.4 | Supply requirements | 32 |
| 4.5 | Testing | 32 |
| 1 | Instruments required 1A, 1B | 32, 33 |
| 2 | Results - Characteristic curves 2A, 2B | 32, 35 |
| 3 | Calibration procedure - TEST POINTS | 35, 38 |
| 4 | Comments - Conclusions | 39 |
| 5. | AC/DC CONVERTER - VERTICAL SCANNING MODULE | 41 |
| 5.1 | Function | 42 |
| 5.2 | Block diagram - Operatioq | 42 |
| 5.3 | Circuit diagram - Operation | 42 |
| 5.3.1 | Analytical cct explanation-Materials Function | 44 |
| 5.4 | Supply requirements | 46 |
| 5.5 | Testing | 46 |
| 1 | Instruments required | 46 |
| 2 | Results - characteristic curves | 46 |
| 3 | Calibration procedure - TEST POINTS | 46 |
| 4 | Comments - Conclusions | 47 |

| | | |
|-------|---|----|
| 6. | STATIC RAM MODULE | 49 |
| 6.1 | Function | 50 |
| 6.2 | Block diagram - Operation | 50 |
| 6.3 | Cct diagram - Operation | 51 |
| 6.3.1 | Analytical cct explanation-Materials Function | 54 |
| 6.4 | Supply requirements | 56 |
| 6.5 | Testing | 56 |
| | 1 Instruments required | 56 |
| | 2 Results - characteristic curves | 56 |
| | 3 Calibration procedure - TEST POINTS | 59 |
| | 4 Comments - Conclusions | 59 |
| 7. | MAIN CHASSIS BOARD | 61 |
| | (Power Supplies - Control Logic - Remote Control | |
| 7.1 | Function | 62 |
| 7.2 | Block diagram - Operation | 62 |
| 7.3 | Cct diagram - Operation | 63 |
| 7.3.1 | Analytical cct explanation-Materials function | 67 |
| 7.4 | Supply requirements | 68 |
| 7.5 | Testing | 68 |
| 7.5.1 | : A -Power Supply | 68 |
| | : B -Synchronising cct | 68 |
| 7.5.2 | TEST POINTS | 69 |
| 7.5.3 | Comments - Conclusions | 69 |
| 8. | COMPLETE CONSTRUCTION - CCT DIAGRAM | 71 |
| 8.1 | Overall test - The instrument Frequency Response | 72 |
| 8.2 | Specifications | 74 |
| 8.3 | Acomodating box | 76 |
| 8.4 | Front panel elements (Brief discription -front view) | 76 |
| 8.5 | Operating instructions | 76 |

| | | |
|------|---|----|
| 9. | IMPROVEMENTS - GENERAL CONCLUSIONS | 81 |
| 9.1 | Linearity and Frequency Responce Errors affecting accuracy. | 82 |
| 9.2 | Comparison of recorded and new response curve - Use of dual trace operation. | 85 |
| 9.3 | Incorporate a distortion analyzer module | 87 |
| 10. | DEMONSTRATION | 89 |
| 10.1 | Testing an ampifler | 90 |
| 10.2 | Testing an equalizer | 91 |
| 10.3 | Testing a filter | 92 |
| 10.4 | Testing a speaker (tweeter, bass) | 93 |

REFERENCES

| | | |
|----------|---|--------------------------|
| APPENDIX | 1 | Printed cct boards |
| >> | 2 | Component list - cost |
| >> | 3 | Relevant subjects |
| >> | 4 | DATA SHEETS |
| >> | 5 | TTT Remote control (R+T) |