

DEVELOPMENT OF AN RS-232 TESTER

by

Parperis Marios

Project Report

Submitted to


the Department of Electrical Engineering  
of Higher Technical Institute

Nicosia, Cyprus

In partial fulfillment of the requirements  
for the diploma of  
TECHNICIAN ENGINEER  
in

ELECTRICAL ENGINEERING

June 1991

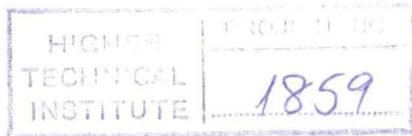

## ACKNOWLEDGMENTS

First I would like to express my sincere thanks to the Cyprus Telecommunication Authority who has sponsored my project.

I would also like to thank my project supervisor Mr. Ch. Theopemptou for his helpful guidance and advice during the design and construction of this project.

Thanks and deep appreciation are hereby expressed to the personnel of the Electronic Laboratory of CY.T.A and especially to the following people:

- Alekos Alexandrou
- Kyriakos Kyllilis

Marios Parperis  
Nicosia June, 1991

## PROJECT SUMMARY

This project deals with the design, construction and testing of an RS-232 tester. The tester will be microprocessor controlled. It will be able to communicate with both DCE and DTE devices.

The tester will also be able to Transmit a standard sequence of characters and Receive or Echo any character. The baud rate of data flow between the tester and the device under test will be rated from 300 to 9600 bits per second. Furthermore the number of stop bits and parity check will be set by the user.

The tester will incorporate a Liquid Crystal Display, a keyboard and some bicolour LEDs in order to provide a multi-task communication to the user.

**PROJECT SUMMARY**

0	Introduction .....	1
---	--------------------	---

**CHAPTER 1 TERMINOLOGY AND PROBLEMS OF RS-232 STANDARD**

1.0	Introduction .....	3
1.1	What is RS-232? .....	3
1.2	Problems associated with RS-232 .....	6

**CHAPTER 2 THE FUNCTIONS OF THE TESTER**

2.0	Introduction .....	8
2.1	Suggested solution for the RS-232 tester .....	8
2.1.1	Monitoring in one direction .....	9
2.1.2	Monitoring in both directions .....	10
2.1.3	Transmitting data .....	11
2.1.4	Echoing data .....	12
2.2	The break out box .....	13

**CHAPTER 3 THE MICROPROCESSOR UNIT**

3.0	Introduction .....	15
3.1	MTB 85-1 specifications .....	15
3.2	The processor .....	15
3.3	The memory .....	17
3.4	The 8155 programmable periferal device .....	18
3.5	Memory Mapping .....	20
3.6	Connectors .....	20

**CHAPTER 4 THE INTERFACE MODULE****Page**

4.0	Introduction .....	22
4.1	The 8251 UART .....	22
4.2	Line drivers and Receivers .....	24
4.3	Interfacing 8251 with the microprocessor .....	25
4.4	Initialising and Testing programs for 8251 ....	30
4.5	Test Results .....	33

**CHAPTER 5 POWER SUPPLIES**

5.0	Introduction .....	34
5.1	Requirements .....	34
5.2	Characteristics - Components Used .....	34

**CHAPTER 6 THE LCD**

6.0	Introduction .....	39
6.1	Specifications .....	39
6.2	Interfacing the LCD .....	40
6.2.1	Input requirements .....	40
6.3	Software used .....	41
6.4	Writing on the display .....	42

7.0	Introduction .....	46
7.1	Interfacing the keyboard with the microprocessor unit .....	46
7.2	Software used .....	47

**CHAPTER 8 SOFTWARE DEVELOPMENT**

8.0	Introduction .....	48
8.1	Program requirements .....	48
8.2	Main Routines used .....	48
8.2.1	Transmitting Routine .....	48
8.2.2	Receiving Routine .....	50
8.2.3	Echo Routine .....	52
8.3	Initialisation .....	52
8.3.1	Baud rate set Routine .....	53
8.4	The flowchart used .....	54
 <b>CONCLUSIONS .....</b>		55
 <b>REFERENCES .....</b>		56