

HIGHER TECHNICAL INSTITUTE

ELECTRICAL ENGINEERING DEPARTMENT

ACADEMIC YEAR 1996/97

MATHCAD APPLICATIONS

Project report submitted by
George Mirson Tsiappas
in part satisfaction of the award
of Diploma of Technician Engineer
in Electrical Engineering of the Higher
Technical Institute, Cyprus

Project Supervisor : Dr. C. Marouchos

External assessor :

Type of project : Individual

Group

June 97.



ABSTRACT

The use of computers is so widespread that complicated calculations, storage of data, designs even experiments are now possible in a much more efficient, faster and easier way than it was several decades ago. All the companies, high schools and Universities today make use of the various software available.

In this work two types of software are examined, presented and used for plotting Bode Diagrams for a number of filters. These are the Mathcad and Electronic Workbench 4.0.

CONTENTS

Acknowledgments	I
Contents	II
Abstract	III
Introduction	IV

CHAPTER 1: Time and Frequency Response: Classical approach

1.0 General	1
1.1 Time Response	1
1.2 Time Response for the first order systems	2
1.3 Time Response for the second order systems	4
1.4 Frequency Response	7
1.5 Bode Diagrams	8
1.6 An example on how we plot Frequency and Time Response curves using the Line Approximation method	13
1.7 How Mathcad can help to plot the Frequency and Time Response curves	17
1.7.1 Mathcad window	17
1.7.2 An example on how Mathcad plots Frequency and Time Response curves	17

CHAPTER 2: Time and Frequency Response using Mathcad

2.0 General	21
2.1 Frequency Response of systems using Mathcad	21
2.1.1 Sallen and Key - High pass filter non-inverting	21
2.1.2 Multiple feedback infinite gain amplifier - Low pass filter	23
2.1.3 Multiple feedback infinite gain amplifier - High pass filter	25
2.1.4 Multiple feedback infinite gain amplifier - Band pass filter	27
2.1.5 Sallen and Key - Low pass filter non-inverting	29
2.1.6 The Integrator	31
2.1.7 Universal filter	33
2.2 Time Response of systems using Mathcad	40
2.2.1 Sallen and Key - High pass filter non-inverting	40
2.2.2 Multiple feedback infinite gain amplifier - Low pass filter	41
2.2.3 Multiple feedback infinite gain amplifier - High pass filter	42
2.2.4 Multiple feedback infinite gain amplifier - Band pass filter	43
2.2.5 Sallen and Key - Low pass filter non-inverting	44
2.2.6 The integrator	45
2.2.7 Universal filter	46

CHAPTER 3: Time and Frequency Response using Electronic Workbench

3.0	General.....	49
3.1	Frequency Response of systems using Electronic Workbench.....	49
3.1.1	Sallen and Key - High pass filter non-inverting.....	49
3.1.2	Multiple feedback infinite gain amplifier - Low pass filter.....	51
3.1.3	Multiple feedback infinite gain amplifier - High pass filter.....	52
3.1.4	Multiple feedback infinite gain amplifier - Band pass filter.....	54
3.1.5	Sallen and Key - Low pass filter non-inverting.....	55
3.1.6	The Integrator.....	57
3.1.7	Universal filter.....	58
3.2	Time Response of systems using Electronic Workbench.....	62
3.2.1	Sallen and Key - High pass filter non-inverting.....	62
3.2.2	Multiple feedback infinite gain amplifier - Low pass filter.....	62
3.2.3	Multiple feedback infinite gain amplifier - High pass filter.....	63
3.2.4	Multiple feedback infinite gain amplifier - Band pass filter.....	63
3.2.5	Sallen and Key - Low pass filter non-inverting.....	64
3.2.6	The Integrator.....	64
3.2.7	Universal filter.....	65

CHAPTER 4: Construction of the Universal filter

4.0	Description of the Universal.....	67
4.1	Experimental test for the Frequency Response of the Universal filter.....	69
4.1.1	Experimental test for the Frequency Response of the Low pass output of the Universal filter.....	70
4.1.2	Experimental test for the Frequency response of the Band pass output of the Universal filter.....	72
4.1.3	Experimental test for the Frequency Response of the High pass output of the Universal filter.....	74

CHAPTER 5: Observations, Discussion, Conclusions and Recommendations

APPENDIX I: Frequency and Time Response of an electronic circuit by employing Mathcad 5.0

APPENDIX II: Frequency and Time Response of an electronic circuit by employing Electronic Workbench 4.0

APPENDIX III: Laplace Transforms pairs.

REFERENCES.